

Week 3 Lab ENGN1218

Week 3 Lab ENGN1218

Bryce Tabangcura
ANU, 01.01.1980

PRELAB QUESTIONS

$$15 - V_x = (5\text{k } \Omega) I_1$$

$$\frac{15 - V_x}{5\text{k } \Omega} = I_1$$

$$V_x = (10\text{k } \Omega) I_2$$

$$\frac{V_x}{10\text{k } \Omega} = I_2$$

$$V_x = (4\text{k } \Omega) I_3$$

$$\frac{V_x}{4\text{k } \Omega} = I_3$$

$$I_1 - I_2 = I_3 - 2 \text{ mA}$$

$$I_1 - I_2 = I_3 - 2 \times 10^{-3}$$

$$\frac{15 - V_x}{5\text{k } \Omega} - \frac{V_x}{10\text{k } \Omega} = \frac{V_x}{4\text{k } \Omega} - 2 \times 10^{-3}$$

$$V_x \approx 9.09$$

$$V_y = V_{ab}$$

$$V = IR$$

$$V_x - 10 = I_1 \times 1$$

$$V_x - 10 = I_1$$

$$V_x - V_y = I_2 \times 1$$

$$V_x - V_{ab} = I_2$$

$$V_y = I_3 \times 1$$

$$V_{ab} = I_3$$

$$KV_{ab} - I_1 = I_2$$

$$I_2 = I_3 - 2A$$

These are all our equations from $V = IR$, now to simultaneously solve

$$V_x - V_{ab} = V_{ab} - 2$$

$$V_x = 2V_{ab} - 2$$

$$KV_{ab} - 2V_{ab} - 2 + 10 = 2V_{ab} - 2 - V_{ab}$$

$$V_{ab} = 14$$

$$V_{ab} = V_y = V_z = 14$$

$$V_x = 2V_{ab} - 2$$

$$V_x = 2 \times 14 - 2$$

$$V_x = 26$$

Now for current through resistors

$$\frac{V}{R} = I$$

$$\frac{V_x - 10}{R_1} = I_1$$

$$\frac{26 - 10}{1} = I_1$$

$$I_1 = 14$$

$$\frac{V_x - V_y}{R_2} = I_2$$

$$\frac{26 - 14}{1} = I_2$$

$$I_2 = 12$$

$$\frac{V_y}{R_3} = I_3$$

$$\frac{14}{1} = I_3$$

$$I_3 = 14$$

find thevenins resistance If you draw the circuit, it ends up being two 1 ohm resistors in series, so

$$1 + 1 = R$$

$$R = 2$$

$$\frac{V}{R} = I$$

$$\frac{14}{2} = I$$

$$I = 7$$